

Mid Sem Question Paper

Name of the program:	B.tech	Semester:	III
Course/Subject Name:	Formal Languages and Automata Theory	Course/Subject Code:	CSE11005
Maximum Marks:	50	Time Duration:	3 Hrs
Total No. of Questions:	18	Total No of Pages:	4

Mid sem question paper

GROUP A(1 X 5)

- 1> The output of an EX-NOR gate is 1. Which input combination is correct? a) $A = 1, B = 0$ b) $A = 0, B = 1$ c) $A = 0, B = 0$ d) $A = 0, B' = 1$.
- 2> A variable on its own or in its complemented form is known as: a) Product Term b) Literal c) Sum Term d) Word
- 3> 3 bits full adder contains a) 3 combinational inputs b) 4 combinational inputs c) 6 combinational inputs d) 8 combinational inputs
- 4> The output of an EX-NOR gate is 1. Which input combination is correct? a) $A = 1, B = 0$ b) $A = 0, B = 1$ c) $A = 0, B = 0$ d) $A = 0, B' = 1$.
- 5> The expression for Absorption law is given by: a) $A + AB = A$ b) $A + AB = B$ c) $AB + AA' =$

A d) $A + B = B + A$

GROUP B(3 X 5)

6> Explain the process of converting SOP to SSOP and POS to SPOS.

7> Classify the logic families based on its operation

8> Explain the major properties of Boolean algebra

