

Mid Sem Question Paper

Name of the program:	B.tech	Semester:	III
Course/Subject Name:	Formal Languages and Automata Theory	Course/Subject Code:	CSE11005
Maximum Marks:	50	Time Duration:	3 Hrs
Total No. of Questions:	18	Total No of Pages:	4

Mid sem question paper

GROUP A(1 X 5)

- 1> A variable on its own or in its complemented form is known as: a) Product Term b) Literal c) Sum Term d) Word
- 2> Which of the following is not a sequential circuit? 1)Flip-Flop 2)Counter 3)Shift register 4)Multiplexer
- 3> The expression for Absorption law is given by: a) $A + AB = A$ b) $A + AB = B$ c) $AB + AA' = A$ d) $A + B = B + A$
- 4> The output of an EX-NOR gate is 1. Which input combination is correct? a) $A = 1, B = 0$ b) $A = 0, B = 1$ c) $A = 0, B = 0$ d) $A = 0, B' = 1$.
- 5> The output of an EX-NOR gate is 1. Which input combination is correct? a) $A = 1, B = 0$ b) $A = 0, B = 1$ c) $A = 0, B = 0$ d) $A = 0, B' = 1$.

GROUP B(3 X 5)

- 6> Explain the major properties of Boolean algebra
- 7> Discuss the classifications of FET devices.
- 8> Classify the logic families based on its operation
-