

Mid Sem Question Paper

Name of the program:	BTech	Semester:	I
Subject Name	Engineering Chemistry-SCY41106	Subject Name	Engineering Chemistry-SCY41106
Maximum Marks:	20	Time Duration:	2 Hrs
Total No. of Questions:	8	Total No of Pages:	2

Mid sem question paper

GROUP A(1 X 5)

- 1> 3 bits full adder contains a)3 combinational inputs b) 4 combinational inputs c)6 combinational inputs d) 8 combinational inputs
- 2> A variable on its own or in its complemented form is known as: a) Product Term b) Literal c) Sum Term d) Word
- 3> Which of the following is not a sequential circuit? 1)Flip-Flop 2)Counter 3)Shift register 4)Multiplexer
- 4> Which of the following is not a sequential circuit? 1)Flip-Flop 2)Counter 3)Shift register 4)Multiplexer
- 5> Which of the following is not a sequential circuit? 1)Flip-Flop 2)Counter 3)Shift register 4)Multiplexer

GROUP B(3 X 5)

- 6> Discuss the classifications of FET devices.
- 7> Discuss the classifications of FET devices.
- 8> Explain the major properties of Boolean algebra
-