

Mid Sem Question Paper

Name of the program:	BTech CSE	Semester:	I
Subject Name	Engineering Mechanics	Subject Code	EME41104
Maximum Marks:	20	Time Duration:	2 Hrs
Total No. of Questions:	8	Total No of Pages:	2

GROUP A(1 X 5)

- 1> 3 bits full adder contains a)3 combinational inputs b) 4 combinational inputs c)6 combinational inputs d) 8 combinational inputs
- 2> The expression for Absorption law is given by: a) $A + AB = A$ b) $A + AB = B$ c) $AB + AA' = A$ d) $A + B = B + A$
- 3> Which of the following is not a sequential circuit? 1)Flip-Flop 2)Counter 3)Shift register 4)Multiplexer
- 4> For example, $3x - 5 = 16$ is an equation.
- 5> The expression for Absorption law is given by: a) $A + AB = A$ b) $A + AB = B$ c) $AB + AA' = A$ d) $A + B = B + A$

GROUP B(3 X 5)

- 6> Classify the logic families based on its operation
- 7> Classify the logic families based on its operation
- 8> Explain the method of Boolean expression minimization using K MAP for 3-variable.

----- The End -----